

# A Stochastic Computational Approach for Accurate and Efficient Reliability Evaluation

A Python Implementation

Jake Humphrey

Department of Electronic and Electrical Engineering  
Imperial College London  
[jbh111@ic.ac.uk](mailto:jbh111@ic.ac.uk)

November 19, 2014

# Reliability of Circuits

Gates in a logic circuit are, alas, not perfect. They are susceptible to error, of which there are three main types:

- ▶ **Stuck-At-One Error:** The output of the gate goes high, regardless of the expected output.
- ▶ **Stuck-At-Zero Error:** The output of the gate goes low, regardless of the expected output.
- ▶ **Von Neumann Error:** The output of the gate becomes the inverse of the expected output.

# Masking Effects

However, there is a chance that errors in one gate will not propagate all the way to an output. This could be due to one of the following *masking effects*

- ▶ **Electrical Masking:** The error does not have a large enough effect on the amplitude of the logic signal to be detected at an input.
- ▶ **Temporal Masking:** The error is input to a latch but occurs at some point in time outside of the latch's detection window.
- ▶ **Logical Masking:** The error does not pass through a multi-input logic gate because the value of the other input(s) fix(es) the output of the gate.